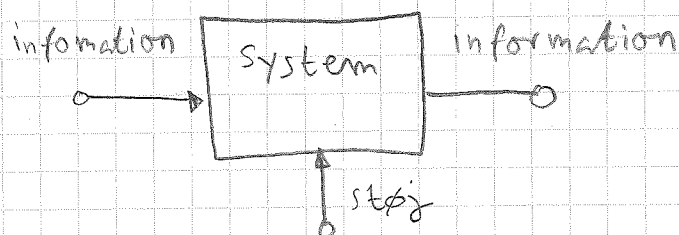
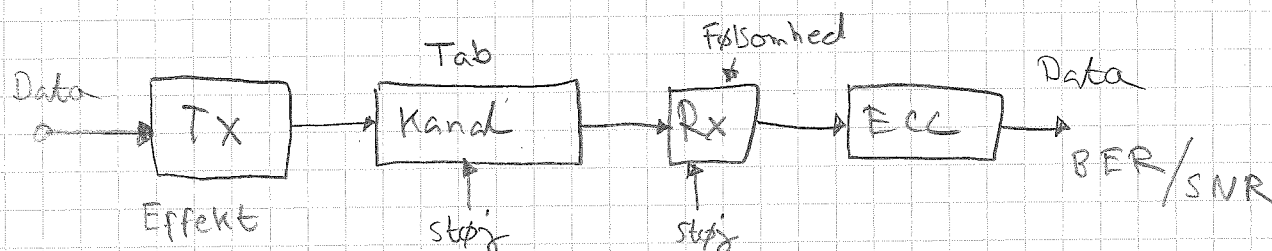


①

Noise Theory - MM1Kommunikationssystemer

BER  
- Bit error rate

ECC  
- Error control coding

Parametre i spil


Bede navn end BER:

BER : Bit Error Probability (BER)

SEP : Symbol — 11 —

FEP : Frame — 1L —

PEP : Packet — 1L —

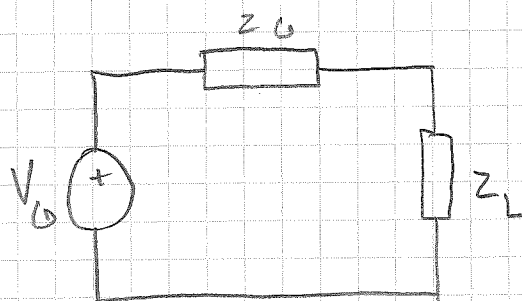Power calculations

For conjugate match

$$(Z_0 = Z_L^*)$$

$$P_{Z_L} = \frac{|V_0|^2}{4 \cdot \text{Re}[Z_L]} \quad [\text{W}]$$

For real impedances ( $Z_L = Z_G = R [\Omega]$ ) we set:

$P_A = \frac{V_G^2}{4 \cdot R} [W] \text{ (or } \frac{V^2}{\Omega})$


$P_A$  = available

and also

$$V_G^2 = 4 \cdot P_A \cdot R [V^2] \text{ (or } W \cdot \Omega)$$

Watts in  $1 \Omega$



For currents we see:

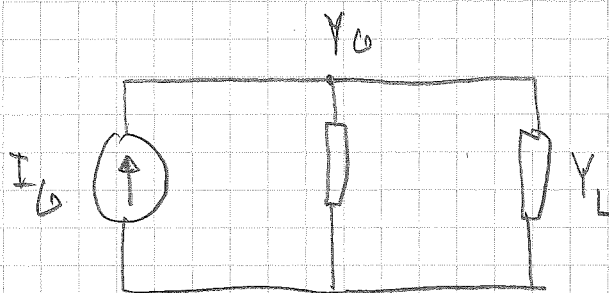


$$I_G^2 = 4 \cdot P_A \cdot G [A^2] \text{ (or } W \cdot S)$$

$$Y_G = Y_L = G$$

### Thermal noise description

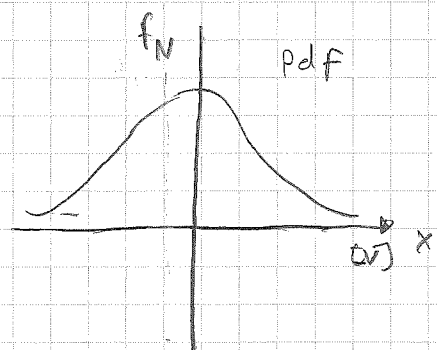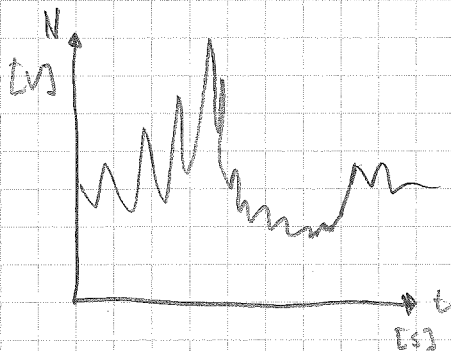

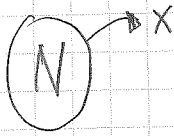Model

Stochastic process

$$f_N(x) = \frac{1}{\sqrt{2\pi}\sigma_N} \cdot e^{-\frac{1}{2} \cdot \frac{(x - \mu_N)^2}{\sigma_N^2}}$$

Statistic moments:

$$E[N] = \int_{-\infty}^{\infty} x f_N(x) dx = \mu_N = 0 \text{ [V]}$$

(mean or average)

$$\text{Var}[N] = E[(N - \mu_N^2)] = E[N^2] = \sigma_N^2 \text{ [V}^2\text{]}$$

(mean square)

$$S_N = \sqrt{\text{Var}[N]} = \sigma_N \text{ [V]}$$

(standard deviation) (root of the mean of the square)

Signal description of random signal
 $\mu_N$ : DC-value,  $\mu_N^2$ : DC-Power

 $\sigma_N$ : AC-value,  $\sigma_N^2$ : AC-power

$$\text{Var}[N] = E[N^2] - \mu_N^2$$

(AC-power) (Total power) (DC-power)

$$E[N^2] = \text{Var}[N] + \mu_N^2$$

Total signal Power AC-power DC-power

Thermal noise

Johnson/Nyquist found that thermal noise is Gaussian with zero mean, and has available power:

$$\Downarrow$$

$$N = kTB \text{ [W]} \text{ or } \left( \frac{V^2}{R} \right)$$

where:

$k$  = Boltzmann's constant [J/K]

$T$  = Temperature [K]

$B$  = Bandwidth [Hz]

Standard temperature  
 (ITRE 1962)

$$T_0 = 290\text{K} (\approx 17^\circ\text{C}) \quad (0\text{K} = -273.16^\circ\text{C})$$

Noise power density

$$N' = \frac{N}{B} = kT \left[ \frac{\text{W}}{\text{Hz}} \right]$$

Noise floor


$$N_0 = kT_0 = 4 \times 10^{-21} \left[ \frac{\text{W}}{\text{Hz}} \right]$$

$$= -174 \text{ [dBm/Hz]}$$

$$= -204 \left[ \frac{\text{dBW}}{\text{Hz}} \right]$$

Noise quantities


- Equivalent noise generator.
- 1L —— resistor.
- Noise temperature.

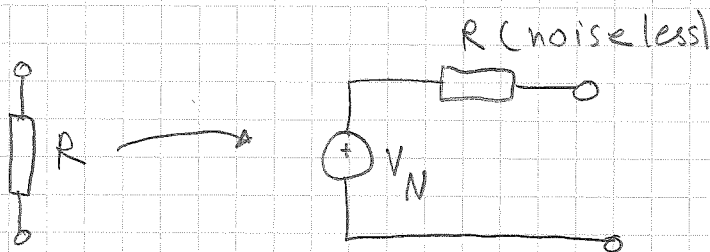Equiv. noise generator

$$V_N^2 = 4 \cdot P_A \cdot R = 4 \cdot N \cdot R$$

$$= 4 \cdot kTB R$$


$$V_N = \sqrt{4kTB R} \text{ [V]}$$

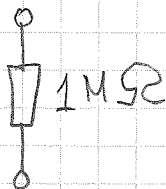Exs. 1


$$290\text{K} \Rightarrow V_N = 18 \mu\text{V}$$

20kHz

# Combining noise generator

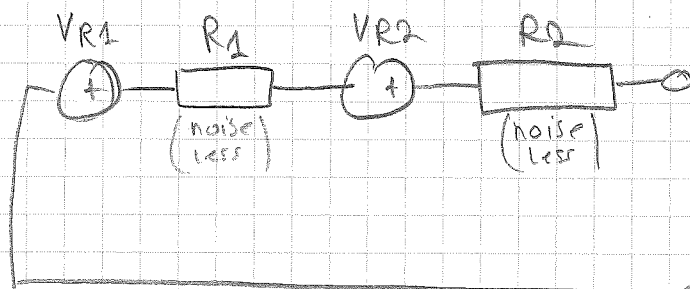

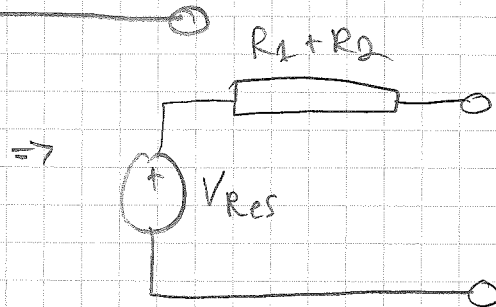Current  
instead of  
voltage  
when  
parallel




$$R_{res} = R_1 + R_2 \text{ [}\Omega\text{]}$$

$$V_{NRES}^2 = V_{N1}^2 + V_{N2}^2$$

$$V_{NRES} = \sqrt{V_{N1}^2 + V_{N2}^2} \text{ [V]}$$


Voltage cannot  
be added due  
to randomness  
could be 1mV  
then 100V

Power does  
not vary  
with time

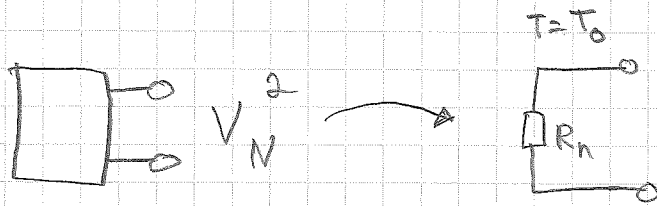Equiv. noise resistor $R_N = G$  when current


$$V_N^2 = 4kTB R = 4kT_0 B R_N [V^2]$$

$$\Rightarrow R_n = \frac{V_N^2}{4kT_0 B R_N} = \frac{V_N^2}{4 \cdot 10^{-6} \cdot B} [\Omega]$$

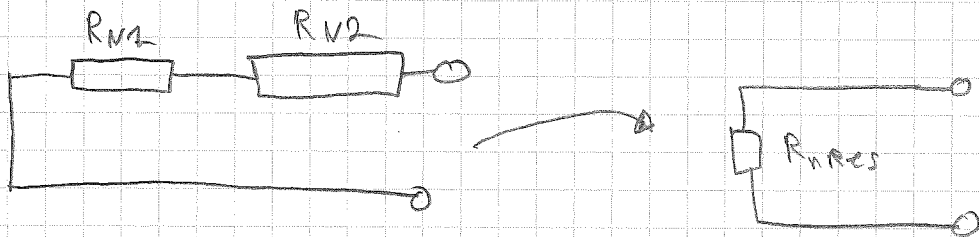Combining noise resistor

$$\begin{aligned} V_{NRES}^2 &= 4kT_0 B R_{N1} + 4kT_0 B R_{N2} \\ &= 4kT_0 B (R_{N1} + R_{N2}) \end{aligned}$$

$$R_{NRES} = R_{N1} + R_{N2} = [\Omega]$$

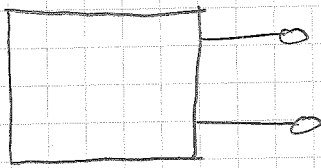Noise temperature

$$T = \frac{N}{k_B} [K]$$

$$T = \frac{N'}{k} [K]$$

$$N = kTB$$

$$N' = kT$$

$$V_N^2 = 4kTBR$$

$$N = kT = \frac{V_N^2}{4kBR} [K]$$




Short-cuts

$$R_N = G$$
  
for current

$$V_N^2 = 4kTBR = 4kT_0 B R_N$$

$$\Rightarrow T/T_0 = R_N/R = G_N/G [.]$$

$$R_N = \text{eq noise resistance}$$

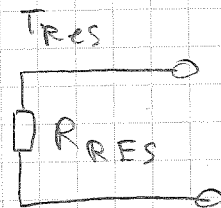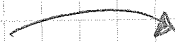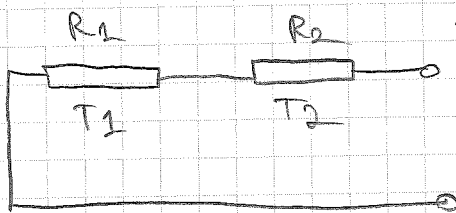Combining components

$$R_{RES} = R_1 + R_2$$

$$R_{RES} = R_{N1} + R_{N2} = R_1 \cdot \frac{T_1}{T_0} + R_2 \cdot \frac{T_2}{T_0}$$

$$= 1/T_0 (T_1 R_1 + T_2 R_2)$$

$$T_{RES} = T_0 \cdot \frac{R_{RES}}{R_{RES}} = \frac{R_1 T_1 + R_2 T_2}{R_1 + R_2}$$



MM1

12/9

⑨

$\Rightarrow$  Co for current and parallel

$$= T_1 \cdot \frac{R_1}{R_1 + R_2} + T_2 \cdot \frac{R_2}{R_1 + R_2} \quad [K]$$