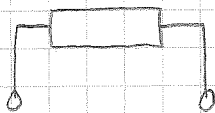


Noise Theory 2 - Noise in two-ports

①

Noise in circuits



1-port

Component

impedance

noise




2-port

Amplifier

Transfer function

Noise factor

Power calculations

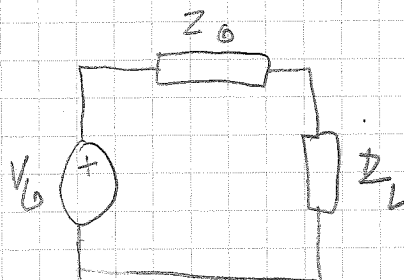


only real parts of impedances produce noise

Available power:

$$P_A = P_{Z_L} \Big|_{Z_L=Z_G} = \frac{|V_G|^2}{4 \cdot R\{Z_G\}} [W]$$

Power gains

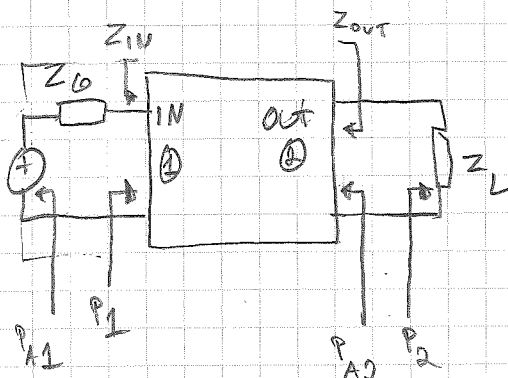

Operating power gain: $G = \frac{P_R}{P_1} \left[\frac{W}{W} = \cdot \right]$ Depends on Z_L and Z_G

Transducer — 11 — : $G_T = \frac{P_2}{P_{A1}} [\cdot]$

Available power gain: $G_A = \frac{P_{A2}}{P_{A1}} \left[\cdot \right]$ Depends on Z_0 (not Z_L)

If $Z_0 = Z_{IN}^*$ ($P_1 = P_{A1}$) then $G_T = G$

If $Z_L = Z_{OUT}^*$ ($P_2 = P_{A2}$) then $G_T = G_A$

If $(Z_0 = Z_{IN}^*) \wedge (Z_L = Z_{OUT}^*)$ then $G_T = G = G_A$

The transducer power gain expresses the advantage of using an amplifier as opposed to matching.

With no amplifier


$$P_{ZL} = P_{A1} \quad (\text{for } Z_0 = Z_L^*)$$

With amplifier

$$P_{ZL} = P_2 = P_{A1} \cdot G_T \quad (\text{Power in load})$$

More on power gains

Blocks in cascade

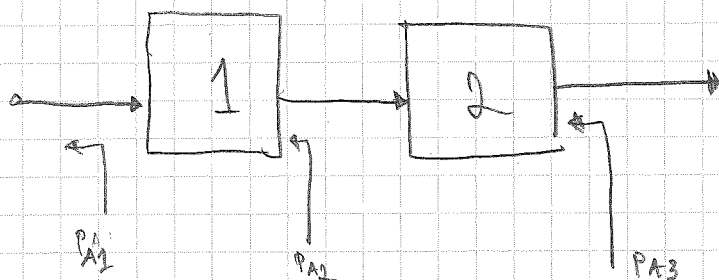


$$G_{A1} = \frac{P_{A2}}{P_{A1}}$$

$$G_2 = \frac{P_{A3}}{P_{A2}}$$

$$G_{AES} = \frac{P_{A3}}{P_{A1}} = \frac{P_{A2}}{P_{A1}} \cdot \frac{P_{A3}}{P_{A2}} = G_{A1} \cdot G_{A2}$$

$$G_{TRES} = \frac{P_3}{P_{A1}} = \frac{P_{A2}}{P_{A1}} \cdot \frac{P_3}{P_{A2}} = G_{A1} \cdot G_{T2}$$

Effective Noise Temperature

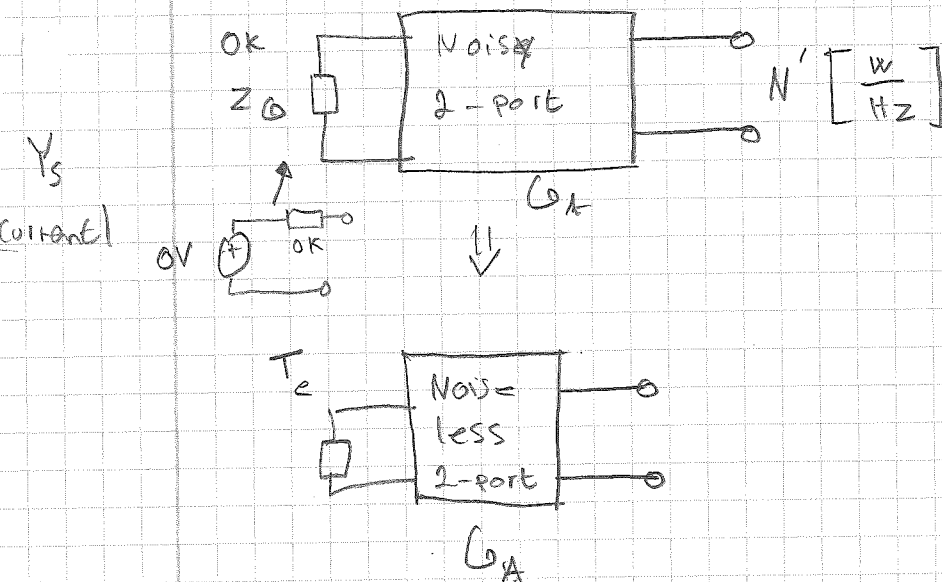

Z_0 is necessary
to calc Available
power

k = noiseless

T_e = effective [K]
noise temp

Noise at the output:

$$N' = k T_e G_A \text{ [W/Hz]}$$

$$N = k T_e B G_A \text{ [W]}$$

Here G_A is constant with respect to frequency

Equivalent noise bandwidth

For G_A not being constant, we write


$$N = kT_e B_N \cdot G_A' = kT_e \int G_A \cdot df$$

We have:


$$B_N \cdot G_A' = \int_{-\infty}^{\infty} |H(f)|^2 df$$

$$B_N = \frac{\int |H(f)|^2 df}{G_A'}$$

G_A' normally would be $G_{A,MAX}$

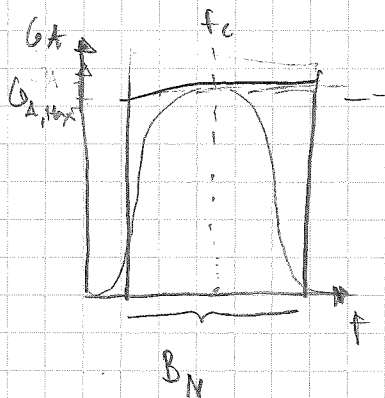

f_c should be specified
sometimes G_T is used

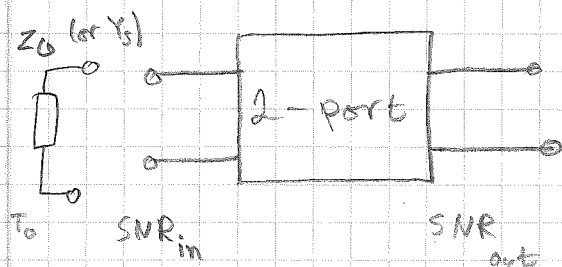Noise factor

The noise factor F expresses the degradation of SNR:

$$F = \frac{SNR_{in}}{SNR_{out}} = \frac{S_{in}/N_{in}}{S_{out}/N_{out}} = \frac{S_{in}}{S_{out}} \cdot \frac{N_{out}}{N_{in}}$$

$$= \frac{1}{G_A} \cdot \frac{N_{out}}{N_{in}} \quad \left. \begin{array}{c} \text{same bandwidth} \\ \text{use } G_A \text{ because of noise signals} \end{array} \right\}$$

where $n = N$:

$$G_A = \frac{S_{out}}{S_{in}} \quad [.]$$

$$N_{in} = kT_0$$


$$N_{out} = kT_0 G_A + kT_e G_A$$

We get:

$$F = \frac{1}{G_A} \cdot \frac{kT_0 G_A + kT_e G_A}{kT_0}$$

$$= 1 + \frac{T_e}{T_0} \quad [.]$$

Illustration

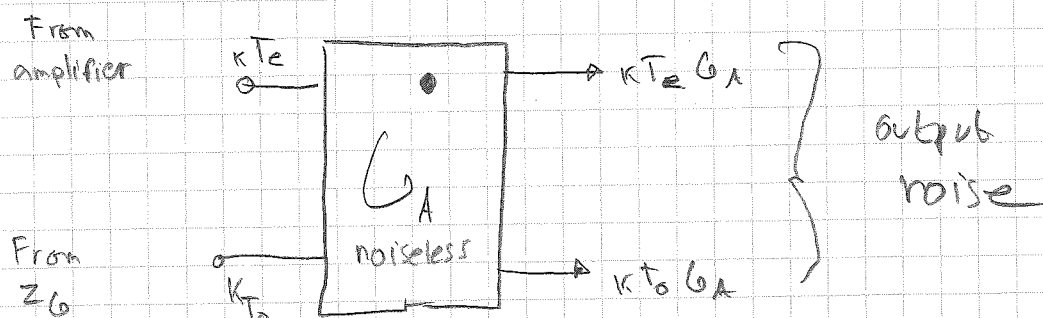

Noise factor cont.

Noise figure:


$$NF = 10 \log F \text{ [dB]}$$

Excess noise ratio (ENR):

$$ENR = F - 1 = \frac{T_e}{T_0} \text{ [°]}$$

leading to:

$$T_e = T_0 \cdot ENR = 290 \cdot ENR \text{ [K]}$$

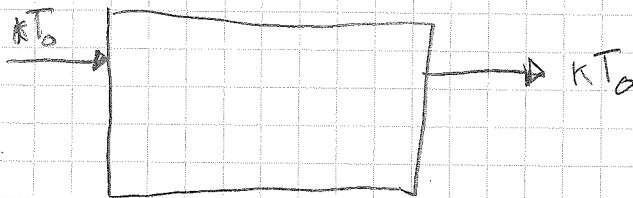Resistive attenuatorNoise factor:


$$F = \frac{1}{G_A} \cdot \frac{N_{out}'}{N_{in}} = \frac{1}{G_A} = L$$

insertion loss

$$T_e = T_0 \cdot (L - 1)$$

EX

Resistive attenuator

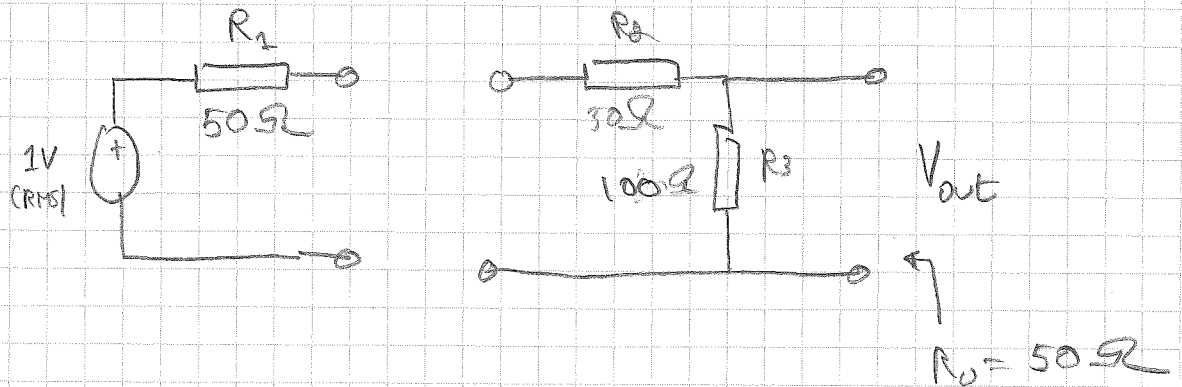

$$V_{out} = 0.5V$$


$$P_{A1} = \frac{V_0^2}{4 \cdot R_1} = \frac{1}{200} = 5mW$$

$$P_{A2} = \frac{V_{out}^2}{4 \cdot R_0} = \frac{1}{2} \cdot \frac{1}{200} = \frac{5}{4} mW$$

$$G_A = \frac{P_{A2}}{P_{A1}} = \frac{1}{4} \Rightarrow L = \frac{1}{G_A} = 4$$



$$F = 4$$

$$NF = 6dB$$

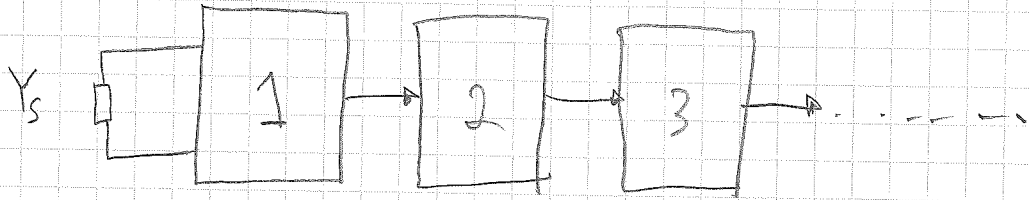Friss cascade formula

The resulting noise factor:

$$F_{RES} = F_1 + \overset{\text{smallest noise factor place}}{\frac{F_2 - 1}{G_{A1}}} + \frac{F_3 - 1}{G_{A1} G_{A2}} + \frac{F_4 - 1}{G_{A1} G_{A2} G_{A3}} + \dots$$

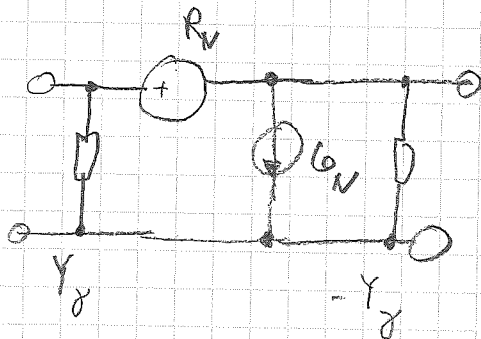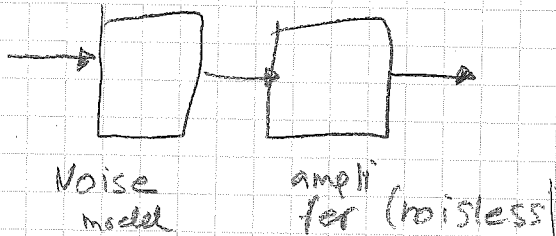Noise parameters

4 values:

$$R_N, G_N, Y_s \quad (R \text{ or } Im)$$